

Exercice 1

1°/ $m = \frac{U_{2V}}{U_{1V}} = \frac{225}{1500} = 0,15$

2°/ $I_a = I_{1V} \cos \varphi_V$ $\cos \varphi_V = \frac{P_{1V}}{U_{1V} I_{1V}}$
 $\cos \varphi_V = \frac{300}{1500 \times 2} = 0,1$
 $\rightarrow I_a = 2 \times 0,1 = 0,2 \text{ A}$

3°/ $P_{JV} = R_1 I_{1V}^2$ $R_1 = \frac{U_1}{I_1} = \frac{2,15}{10} = 0,215 \Omega$
 $P_{JV} = 0,215 \times 2^2 = 0,86 \text{ W}$ essai en court-circuit
 $P_{JV} \ll P_{1V} = P_{FV}$

4°/ $P_{FV} = \alpha \times U_1^2$
 Lors de l'essai en court-circuit: $P_{FVcc} = \alpha U_{1cc}^2$
 " " à vide: $P_{FVv} = \alpha U_{1v}^2$

$\Rightarrow \alpha = \frac{P_{FVv}}{U_{1v}^2} = \frac{300}{1500^2} = 133 \cdot 10^{-6} \text{ S}$

ce qui nous permet de calculer P_{FVcc}
 $P_{FVcc} = \alpha U_{1cc}^2 = 133 \cdot 10^{-6} \times 225^2 =$

$P_{FVcc} = 0,0675 \text{ W}$

autre méthode: à vide $P_{FVv} = \alpha \times U_{1v}^2$
 en court-circuit $P_{FVcc} = \alpha U_{1cc}^2$

$\Rightarrow \frac{P_{FVcc}}{P_{FVv}} = \frac{\alpha U_{1cc}^2}{\alpha U_{1v}^2} = \left(\frac{U_{1cc}}{U_{1v}} \right)^2 \Rightarrow$


$P_{FVcc} = P_{FVv} \times \left(\frac{U_{1cc}}{U_{1v}} \right)^2$

AN: $P_{FVcc} = 300 \times \left(\frac{225}{1500} \right)^2 \approx 0,0675 \text{ W}$

5°/ $R_s = \frac{P_{1cc}}{I_{2cc}^2}$ avec $I_{2cc} = \frac{I_{1cc}}{m} = \frac{225 \cdot 150}{0,15} \text{ A}$

$R_s = \frac{225}{150^2} = 10 \text{ m}\Omega$; $Z_s = \frac{m U_{1cc}}{I_{2cc}} = \frac{0,15 \times 225}{150}$

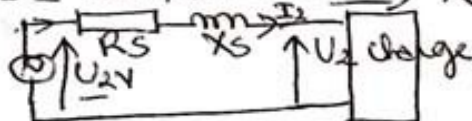$Z_s = 22,5 \text{ m}\Omega \Rightarrow X_s = \sqrt{Z_s^2 - R_s^2} = 20,15 \text{ m}\Omega$



$$6^o) \quad U_1 = 1500V;$$

$$I_2 = 200A$$

$$a) \quad \varphi_2 = (\vec{I}_2, \vec{U}_2)$$

$$\Delta U_2 \approx R_S I_2 \cos \varphi_2 + X_S I_2 \sin \varphi_2 = 0$$

$$\Rightarrow R_S I_2 \cos \varphi_2 = -X_S I_2 \sin \varphi_2$$

$$\Rightarrow R_S \cos \varphi_2 = -X_S \sin \varphi_2$$

$$\Rightarrow \frac{R_S}{X_S} = -\frac{\sin \varphi_2}{\cos \varphi_2} = -\tan \varphi_2 \Rightarrow \boxed{\tan \varphi_2 = -\frac{R_S}{X_S}}$$

$$\text{AN: } \tan \varphi_2 = -\frac{10}{20,15} = -0,496$$

$$\varphi_2 = \tan^{-1}(-0,496) = -26,38^\circ$$

il faut une charge capacitive de facteur de puissance

$$\cos \varphi_2 = \cos(-26,38) = 0,895$$

$$b) \quad \frac{\Delta U_2}{U_2} \% ?$$

$$\Delta U_2 \% = \frac{100(U_{2V} - U_2)}{U_{2V}} = \frac{\Delta U_2}{U_{2V}} \times 100$$

$$\Delta U_2 = R_S I_2 \cos \varphi_2 + X_S I_2 \sin \varphi_2$$

$$\varphi_2 = \cos^{-1}(0,895) = 26,38^\circ \Rightarrow \sin \varphi_2 = 0,44$$

$$\Delta U_2 = 10 \cdot 10^3 \times 200 \times 0,895 + 20,15 \cdot 10^3 \times 200 \times 0,44$$

$$\Delta U_2 = 4V \Rightarrow \frac{\Delta U_2}{U_{2V}} = \frac{4}{225} \times 100 = 1,77\%$$

$$\boxed{\Delta U_2 \% = 1,77\%}$$

$$\eta = \frac{P_2}{P_1} \quad \text{avec } P_1 = P_{\text{re}} + P_{\text{r}} + P_S$$

$$P_2 = U_2 I_2 \cos \varphi_2$$

$$U_2 = U_{2V} - \Delta U_2 = 225 - 4 = 221V$$

$$P_2 = 221 \times 200 \times 0,895 = 39460W$$

$$P_1 = 39460 + 300 + 225 = 39785W$$

$$\eta = \frac{39460}{39785} = 99,18\%$$

Exercice 2:

1°/ $\cos \varphi = \cos 36^\circ = 0,809$

2°/ La tension nominale d'un enroulement du stator est 400V, cette tension correspond à la tension composée du réseau \Rightarrow on couple le stator du moteur en TRIANGLE.

3°/ $J = \frac{U}{Z} = \frac{400}{4615} = 8,6 \text{ A}$

4°/ $I = J \times \sqrt{3} = 8,6 \times \sqrt{3} = 14,9 \text{ A}$

5°/ $S = U I \sqrt{3} = 400 \times 14,9 \times \sqrt{3} = 10322 \text{ W}$


6°/ $P = U I \sqrt{3} \cos \varphi = 400 \times 14,9 \times \sqrt{3} \times 0,809$
 $P = 8350 \text{ W}$

7°/ $Q = P \times \tan \varphi = 8350 \times \tan 36^\circ = 6066 \text{ Var}$

$(Q = \sqrt{S^2 - P^2} = \sqrt{10322^2 - 8350^2} = 6066 \text{ Var})$

exercice 3

1°/

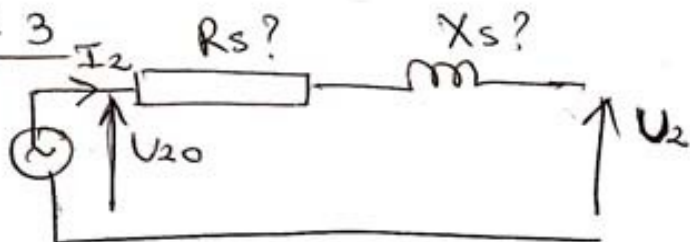

$$R_s = \frac{P_{1cc}}{I_{2cc}^2} = \frac{1000}{200^2} = 25 \text{ m}\Omega$$

$$Z_s = \frac{m U_{1cc}}{I_{2cc}} = \frac{0.1045 \times 250}{200} = 56,25 \text{ m}\Omega$$

$$m = \frac{U_{20}}{U_1} = \frac{225}{5000} = 0.1045$$

$$X_s = \sqrt{Z_s^2 - R_s^2} = \sqrt{56,25^2 - 25^2} = 50,39 \text{ m}\Omega$$

2°/ U_2 ? $\Delta U_2 = R_s I_2 \cos \varphi_2 + X_s I_2 \sin \varphi_2$

$$\cos \varphi_2 = 0.18 \Rightarrow \varphi_2 = + \cos^{-1}(0.18) = 36,86^\circ$$

$$\sin \varphi_2 = \sin 36,86 = 0.16$$

$$\Delta U_2 = 25 \cdot 10^{-3} \times 180 \times 0.18 + 56,25 \cdot 10^{-3} \times 180 \times 0.16$$

$$\Delta U_2 = 9,675 \text{ V}$$

$$U_2 = U_{20} - \Delta U_2 = 225 - 9,675 = 215,325 \text{ V}$$

Pertes Joule: P_J ?

$$\left. \begin{aligned} P_{1cc} &= R_s I_{2cc}^2 \\ P_J &= R_s I_2^2 \end{aligned} \right\} \frac{P_J}{P_{1cc}} = \frac{R_s I_2^2}{R_s I_{2cc}^2} = \left(\frac{I_2}{I_{2cc}} \right)^2$$

$$P_J = P_{1cc} \times \left(\frac{I_2}{I_{2cc}} \right)^2 = 1000 \times \left(\frac{180}{200} \right)^2$$

$$P_J = 810 \text{ W}$$

Pertes Joule pour $I_2 = 180 \text{ A}$

2°/ $\eta = \frac{P_2}{P_1} = \frac{P_2}{P_2 + P_{PF} + P_J}$

$P_{PF} = P_{10} = 790 \text{ W}$
 car tension primaire
 identique que
 lors del essai vide

$$P_2 = U_2 I_2 \cos \varphi_2 = 215,325 \times 180 \times 0.18 = 31006 \text{ W}$$

$$P_1 = 31006 + 790 + 810 = 32606 \text{ W}$$

$$\eta = \frac{31006}{32606} = 95\%$$

exercice 4

$$1^{\circ} / N_1 = \frac{N_2}{m} \quad m = \frac{U_{20}}{U_{10}} = \frac{700}{10.000} = 0,07$$

$$N_1 = \frac{595}{0,07} = 8500 \text{ spires}$$

$$2^{\circ} / U_2 ? \text{ pour } I_2 = 400 \text{ A}$$

avec $\cos \varphi_2 = 0,18$ quand $U_1 = 10 \text{ kV}$
 $U_2 = U_{20} - \Delta U_2$ et $\Delta U_2 = R_s I_2 \cos \varphi_2 + X_s I_2 \sin \varphi_2$
il faut calculer les valeurs de R_s et de X_s :

$$R_s = \frac{P_{1cc}}{I_{2cc}^2} = \frac{8000}{400^2} = 5 \text{ m}\Omega$$

$$Z_s = \frac{m U_{1cc}}{I_{2cc}} = \frac{0,07 \times 10000}{400} = 17,5 \text{ m}\Omega$$

$$X_s = \sqrt{Z_s^2 - R_s^2} = \sqrt{17,5^2 - 5^2} = 16,717 \text{ m}\Omega$$

Calcul de la chute de tension: $\sin \varphi = \sqrt{1 - \cos^2 \varphi} = \sqrt{1 - 0,18^2} = 0,986$

$$\Delta U_2 = 5 \cdot 10^{-3} \times 400 \times 0,18 + 16,717 \cdot 10^{-3} \times 400 \times 0,986$$

$$\Delta U_2 = 56,25 \text{ V} \Rightarrow U_2 = U_{20} - \Delta U_2 = 700 - 56,25$$

$$U_2 = 643,75 \text{ V}$$

$$\text{Pour } I_2 = 200 \text{ A} \quad \Delta U_2 = R_s I_2 \cos \varphi_2 + X_s I_2 \sin \varphi_2$$

$$\Delta U_2 = 5 \cdot 10^{-3} \times 200 \times 0,18 + 16,717 \cdot 10^{-3} \times 200 \times 0,986 = 28,125 \text{ V}$$

$$P_2 = U_2 I_2 \cos \varphi_2 = (U_{20} - \Delta U_2) I_2 \cos \varphi_2 = (700 - 28,125) \times 200 \times 0,18$$

$$P_2 = 10715 \text{ kW}$$

$$P_1 = P_2 + P_{Fe} + P_J \quad \text{pour } I_2 = 200 \text{ A} \Rightarrow P_J = P_{1cc} \times \left(\frac{I_2}{I_{2cc}} \right)^2$$

$$P_J = 8000 \times \left(\frac{200}{400} \right)^2 = 2000 \text{ W}$$

$$P_{Fe} = P_{10} = 6900 \text{ W, car on a la même tension primaire}$$

$$P_1 = 10715 + 2 + 6,9 = 11614 \text{ kW}$$

$$\eta = P_2 / P_1 = \frac{10715}{11614} = 92,35\%$$

Exercice 5:


10/

a) $\cos \varphi = \frac{P_{1V}}{S_{1V}} = \frac{P_{1V}}{U_{1V} I_{1V}} = \frac{36}{220 \times 0,13} = 0,1545$

b) $N_2 = m \times N_1 = \left(\frac{U_{2V}}{U_1}\right) \times N_1 = \frac{110 \times 500}{220} = 250 \text{ spires}$

27/

a)

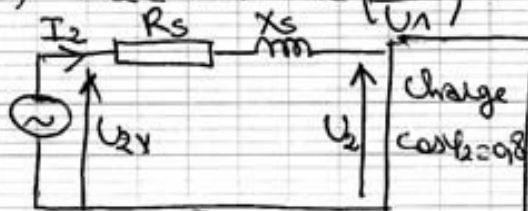

modèle équivalent de Thévenin du transformateur, vu du secondaire

$$\vec{U}_{2V} = R_s \vec{I}_2 + X_s \vec{I}_2 + \vec{U}_2$$

- calcul des éléments du modèle équivalent:

$$R_s = \frac{P_{1cc}}{I_{2cc}^2} = \frac{30}{10^2} = 300 \text{ m}\Omega$$

$$Z_s = m \frac{U_{1cc}}{I_{2cc}} = 0,15 \times \frac{10}{10} = 500 \text{ m}\Omega$$

$$X_s = \sqrt{Z_s^2 - R_s^2} = 400 \text{ m}\Omega$$

Construction de Fresnel: $R_s I_2 = 0,13 \times 20 = 6 \text{ V}$

$X_s I_2 = 0,14 \times 20 = 8 \text{ V}$, $U_{2V} = 110 \text{ V}$

$\varphi_2 = (\vec{I}_2, \vec{U}_2) = \cos^{-1}(0,18) = 36,86^\circ$

Echelle: 1cm \rightarrow 10cm


arc de cercle de centre O et de rayon U_{2V}

- $R_s I_2 \rightarrow 0,6 \text{ cm}$
- $X_s I_2 \rightarrow 0,8 \text{ cm}$
- $U_{2V} \rightarrow 11 \text{ cm}$

$U_2 = AB \times 10 \text{ V/cm}$

$U_2 = 10 \times 10 \text{ V/cm}$

$U_2 = 100 \text{ V}$

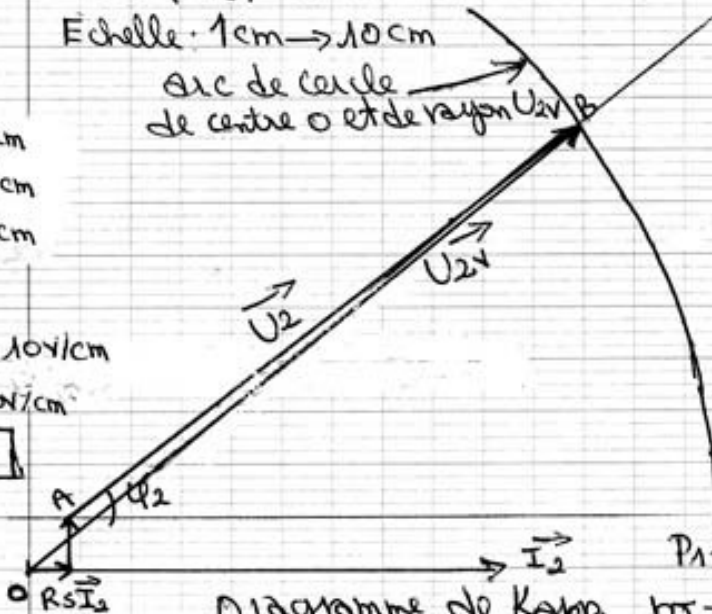

b/

$\Delta U_2 = U_{2V} - U_2 = 110 - 100$

$\Delta U_2 = 10 \text{ V}$

$\Delta U_2 \% = \frac{\Delta U_2 \times 100}{U_{2V}}$

$\Delta U_2 \% = \frac{10 \times 100}{110} = 9\%$

3/ $P_2 = U_2 I_2 \cos \varphi_2$

$P_2 = 100 \times 20 \times 0,8 = 1600 \text{ W}$

$P_1 = P_2 + P_F + P_J$

$P_J = P_{1cc} \left(\frac{I_2}{I_{2cc}}\right)^2 = 30 \times \left(\frac{20}{10}\right)^2$

$P_J = 120 \text{ W}$; $P_1 = 1600 + 36 + 120 = 1756 \text{ W}$

$\eta = \frac{P_2}{P_1} = \frac{1600}{1756} = 91,11\%$